



Fig. 3.25 Block diagram of n-bit parallel adder

Implemented n bit adder using full adder module implemented in previous question.

-The starting carry is 0.

-Then the carry is forwarded ahead in the loop.

-The default N is 64, it is configurable by just changing N in the code.

-The loop is run N times till all the sum and carry are calculated.