

Half Adder circuit


In this program there are 2 inputs inputBit1 and inputBit2 and two outputs sum and carry.

According to the truth table of half adder. Sum is xor of a and b and carry is and of a and b.


These values are assigned to respective output.

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table

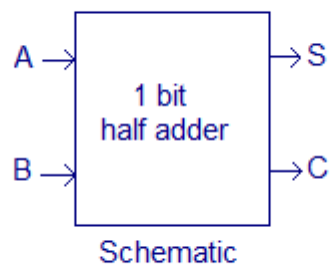

Schematic

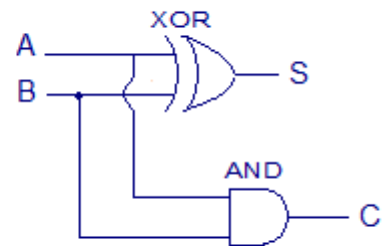

Realization